

# Behavioral HDL

# Recall: Two Main Styles of HDL Implementation

---

- **Structural (Gate-Level)**
  - The module body contains **gate-level description** of the circuit
  - Describe how modules are interconnected
  - Each module contains other modules (instances)
  - ... and interconnections between those modules
  - Describes a hierarchy of modules defined as gates
- **Behavioral**
  - The module body contains **functional description** of the circuit
  - Contains logical and mathematical **operators**
  - **Level of abstraction is higher than gate-level**
    - Many possible gate-level realizations of a behavioral description
- **Many practical designs use a combination of both**

# Behavioral HDL: Defining Functionality

---

```
module example (a, b, c, y);
    input a;
    input b;
    input c;
    output y;


    // here comes the circuit description
    assign y = ~a & ~b & ~c |
                a & ~b & ~c |
                a & ~b &  c;

endmodule
```
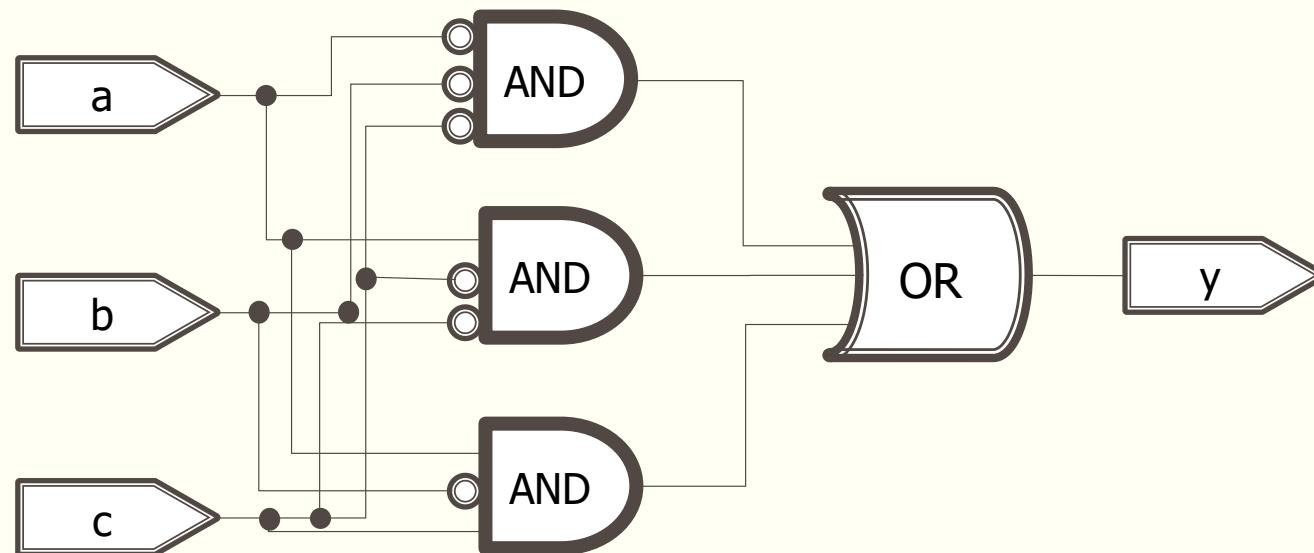
# Behavioral HDL: Schematic View

---

A behavioral implementation still models a hardware circuit!



# Bitwise Operators in Behavioral Verilog

---

```
module gates(input [3:0] a, b,
              output [3:0] y1, y2, y3, y4, y5);


    /* Five different two-input logic
       gates acting on 4 bit buses */

    assign y1 = a & b;      // AND
    assign y2 = a | b;      // OR
    assign y3 = a ^ b;      // XOR
    assign y4 = ~(a & b);  // NAND
    assign y5 = ~(a | b);  // NOR

endmodule
```

# Bitwise Operators: Schematic View

---

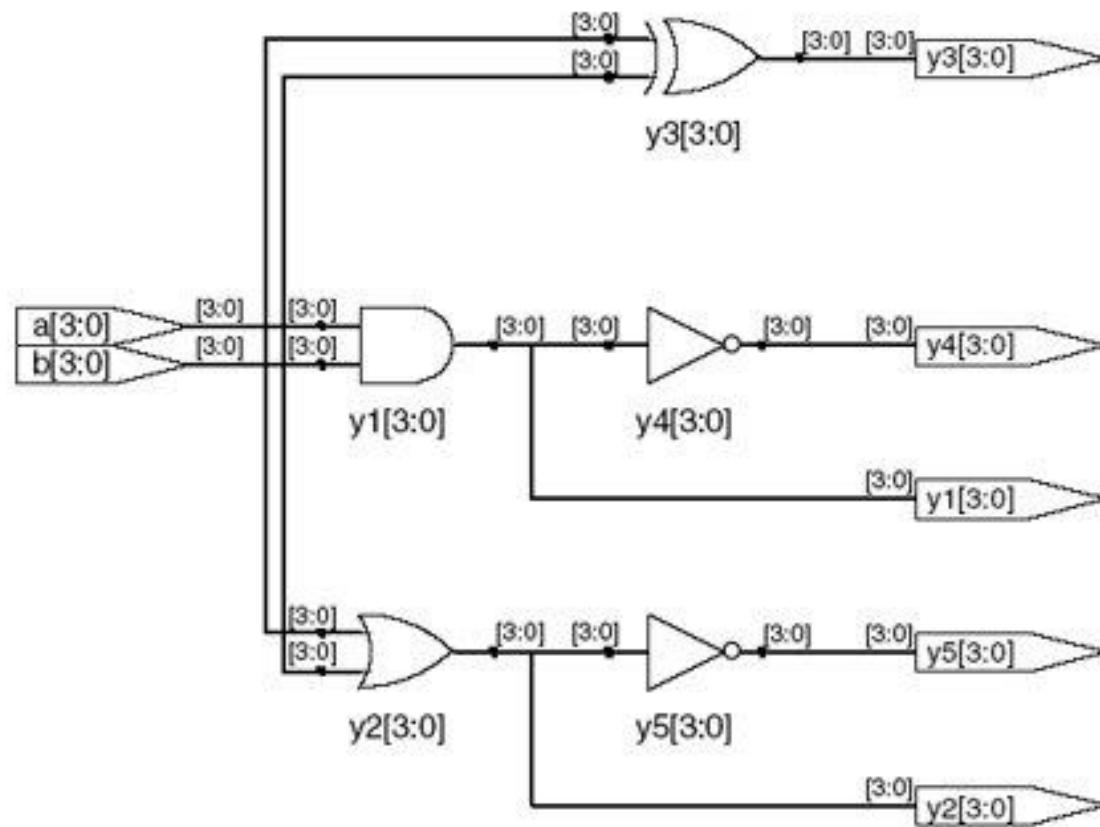

# Reduction Operators in Behavioral Verilog

---

```
module and8(input [7:0] a,
             output      y);


    assign y = &a;

    // &a is much easier to write than
    // assign y = a[7] & a[6] & a[5] & a[4] &
    //           a[3] & a[2] & a[1] & a[0];

endmodule
```

# Reduction Operators: Schematic View

---

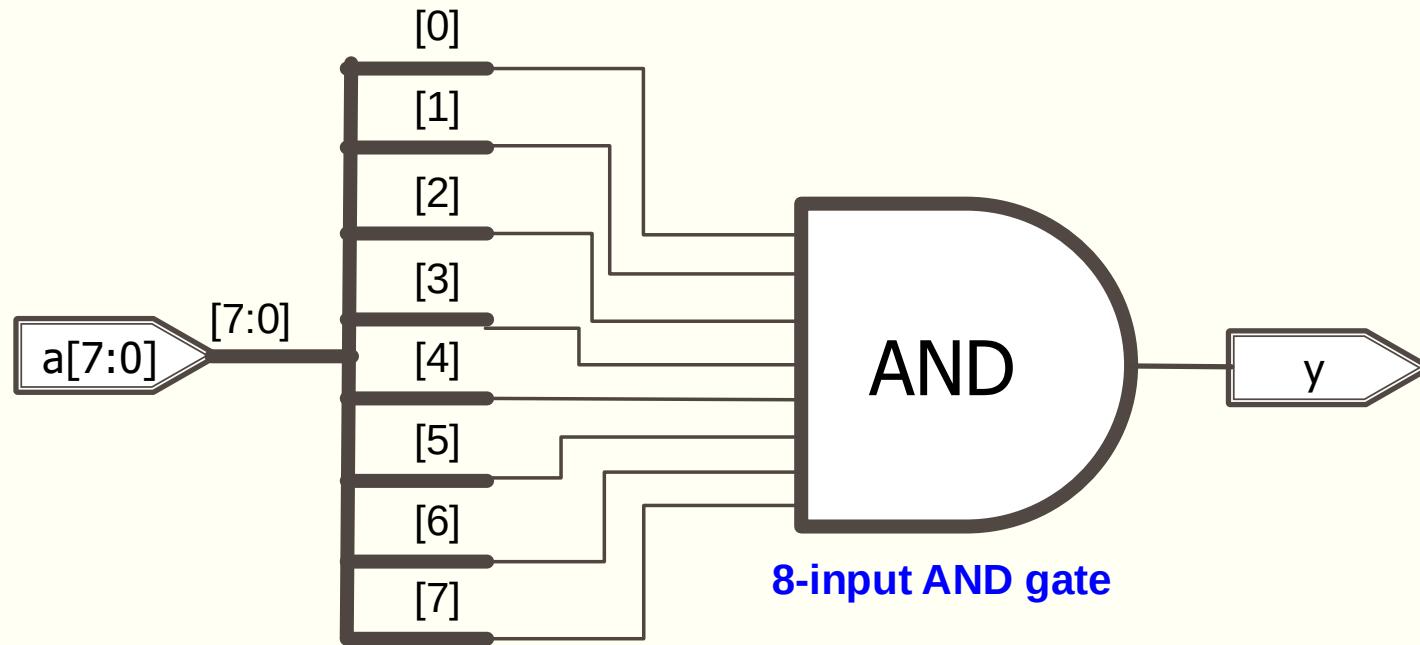

# Conditional Assignment in Behavioral Verilog

---

```
module mux2(input [3:0] d0, d1,
             input      s,
             output [3:0] y);


    assign y = s ? d1 : d0;
    // if (s) then y=d1 else y=d0;

endmodule
```

- ?: is also called a **ternary operator** as it operates on three inputs:
  - s
  - d1
  - d0

# Conditional Assignment: Schematic View

---

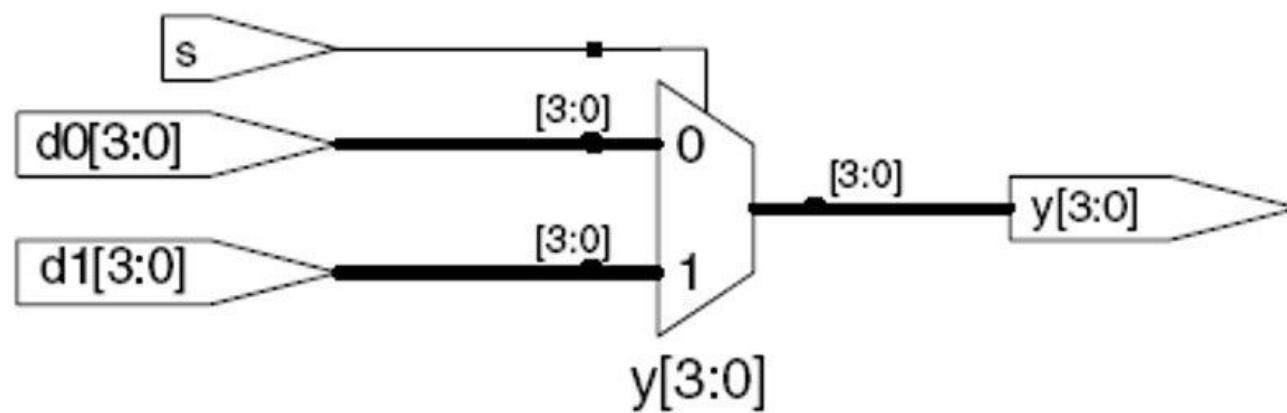

# More Complex Conditional Assignments

---

```
module mux4(input [3:0] d0, d1, d2, d3
            input [1:0] s,
            output [3:0] y);

    assign y = s[1] ? ( s[0] ? d3 : d2)
                  : ( s[0] ? d1 : d0);
    // if (s1) then
    //     if (s0) then y=d3 else y=d2
    // else
    //     if (s0) then y=d1 else y=d0

endmodule
```

# Even More Complex Conditional Assignment

---

```
module mux4(input [3:0] d0, d1, d2, d3
            input [1:0] s,
            output [3:0] y);

    assign y = (s == 2'b11) ? d3 :
                (s == 2'b10) ? d2 :
                (s == 2'b01) ? d1 :
                d0;
    // if      (s = "11" ) then y= d3
    // else if (s = "10" ) then y= d2
    // else if (s = "01" ) then y= d1
    // else                      y= d0

endmodule
```

# Precedence of Operations in Verilog

---

---

**Highest**

|              |                  |
|--------------|------------------|
| ~            | NOT              |
| *, /, %      | mult, div, mod   |
| +, -         | add,sub          |
| <<, >>       | shift            |
| <<<, >>>     | arithmetic shift |
| <, <=, >, >= | comparison       |
| ==, !=       | equal, not equal |
| &, ~&        | AND, NAND        |
| ^, ~^        | XOR, XNOR        |
| , ~          | OR, NOR          |
| ?:           | ternary operator |

**Lowest**

# How to Express Numbers?

---

**N' Bxx**  
**8' b0000\_0001**

- **(N) Number of bits**
  - Expresses how many bits will be used to store the value
- **(B) Base**
  - Can be b (binary), h (hexadecimal), d (decimal), o (octal)
- **(xx) Number**
  - The value expressed in base
  - Can also have X (invalid) and Z (floating), as values
  - Underscore \_ can be used to improve readability

# Number Representation in Verilog

---

| Verilog      | Stored Number | Verilog | Stored Number  |
|--------------|---------------|---------|----------------|
| 4'b1001      | 1001          | 4'd5    | 0101           |
| 8'b1001      | 0000 1001     | 12'hFA3 | 1111 1010 0011 |
| 8'b0000_1001 | 0000 1001     | 8'o12   | 00 001 010     |
| 8'bxX0X1zZ1  | XX0X 1ZZ1     | 4'h7    | 0111           |
| 'b01         | 0000 .. 0001  | 12'h0   | 0000 0000 0000 |

**32 bits  
(default)**

# Floating Signals (Z)


---

- **Floating signal:** Signal that is not driven by any circuit
  - Open circuit, floating wire
- Also known as: **high impedance, hi-Z, tri-stated** signals

```
module tristate_buffer(input [3:0] a,
                      input          en,
                      output [3:0] y);

    assign y = en ? a : 4'bz;


endmodule
```

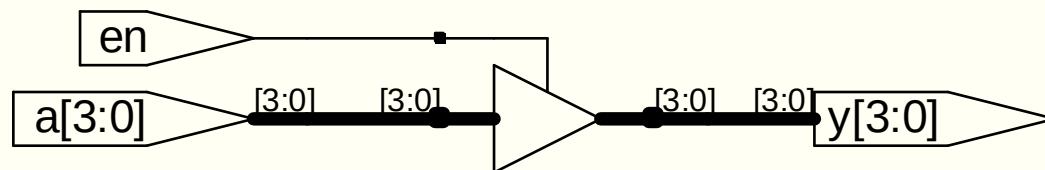
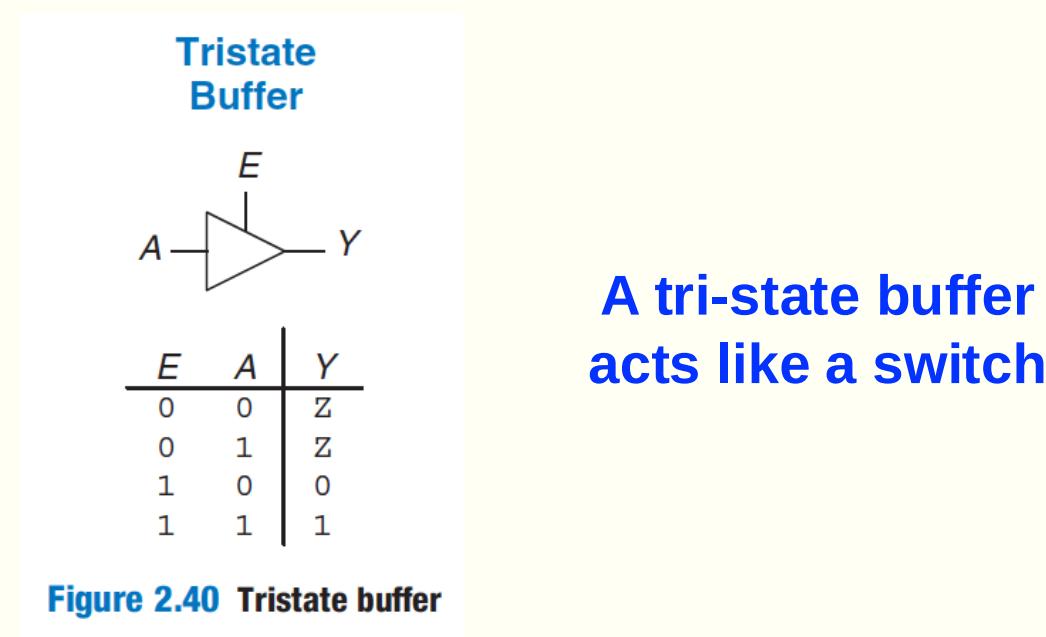
# Tri State Buffer

---

- A tri-state buffer enables gating of different signals onto a wire



- **Floating signal (Z):** Signal that is not driven by any circuit
  - Open circuit, floating wire


## Example: Use of Tri-State Buffer

---

- Imagine a wire connecting the CPU and memory
  - At any time only the CPU or the memory can place a value on the wire, both not both
  - You can have two tri-state buffers: one driven by CPU, the other memory; and ensure at most one is enabled at any time


# Example Design with Tri-State Buffer

---

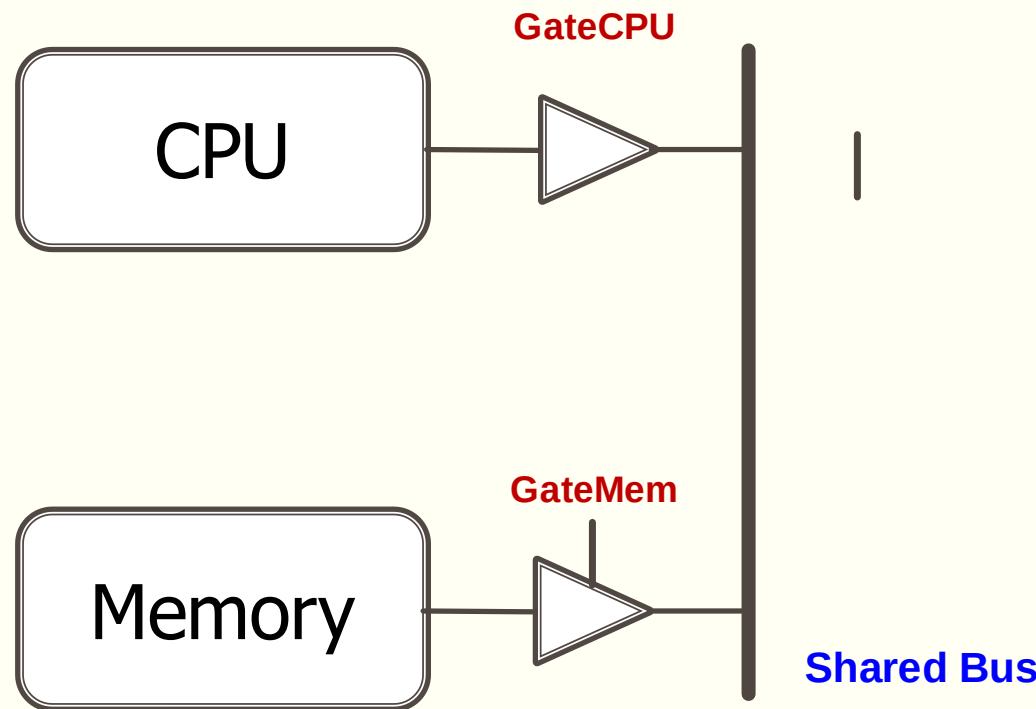

# Another Example

---

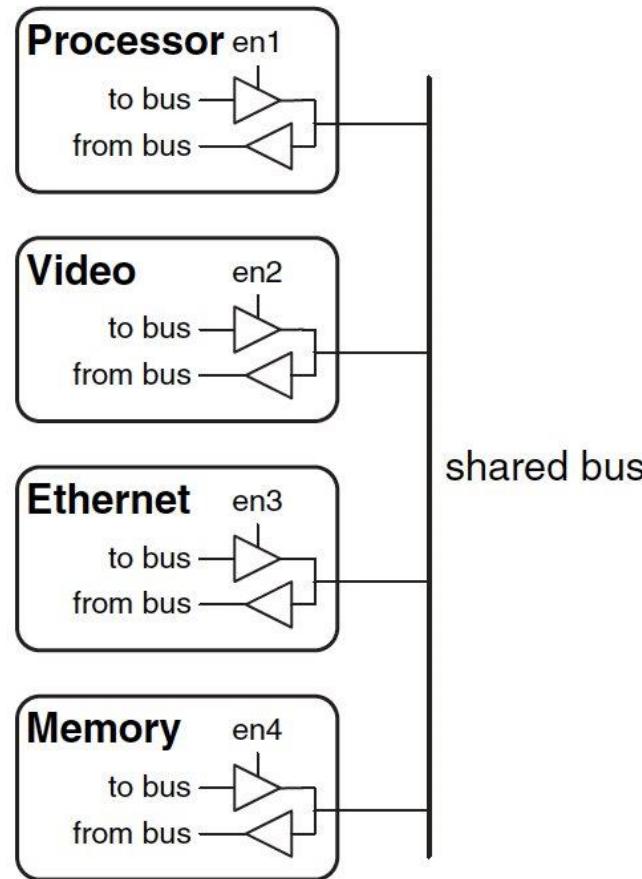

# What Happen with HDL Code?

---

## ■ **Synthesis (i.e., Hardware Synthesis)**

- Modern tools are able to map *synthesizable HDL code* into low-level *cell libraries* → *netlist describing gates and wires*
- They can perform many *optimizations*
- ... however they **can not guarantee** that a solution is optimal
  - Mainly due to *computationally expensive placement* and *routing* algorithms
  - Need to describe your circuit in HDL in a nice-to-synthesize way
- Most common way of Digital Design these days

## ■ **Simulation**

- Allows the behavior of the circuit to be **verified** without actually manufacturing the circuit
- Simulators can work on *structural* or *behavioral* HDL
- Simulation is essential for functional and timing verification

## Recall "This Example"

---


```
module example (a, b, c, y);
    input a;
    input b;
    input c;
    output y;

    // here comes the circuit description
    assign y = ~a & ~b & ~c |
                a & ~b & ~c |
                a & ~b &   c;

endmodule
```



# Synthesizing the "Example"

---

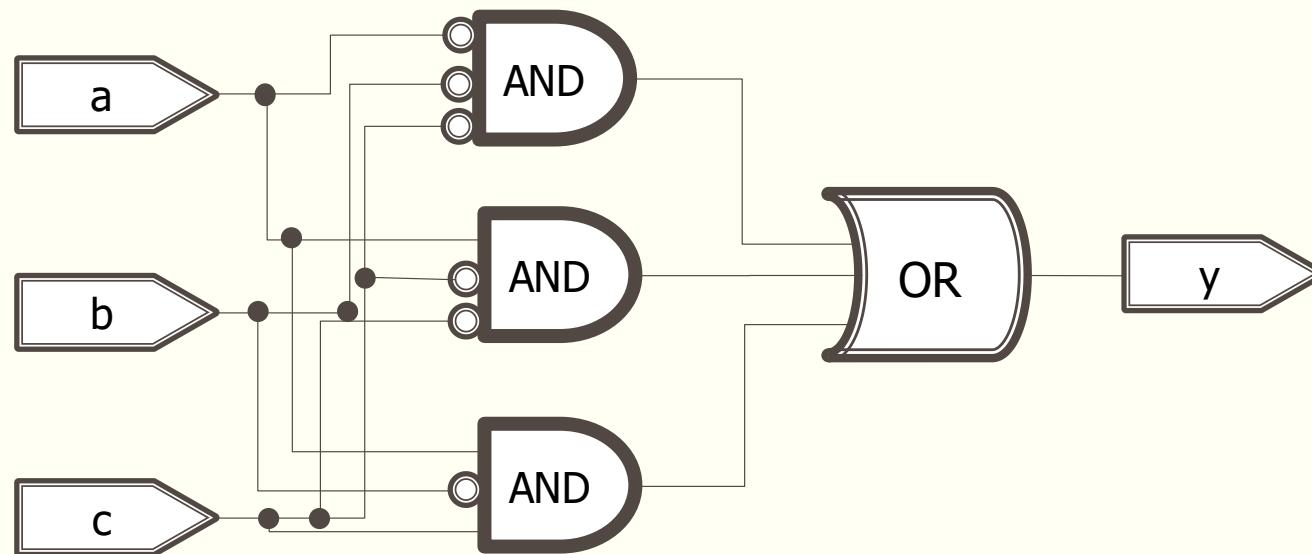

# Simulating the "example"

---

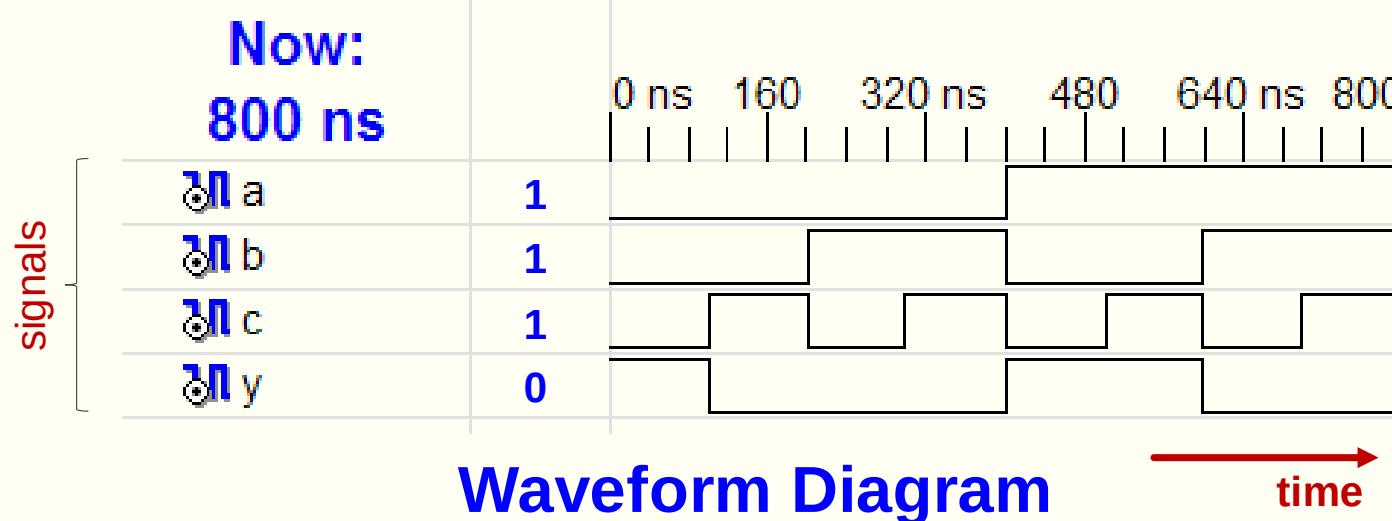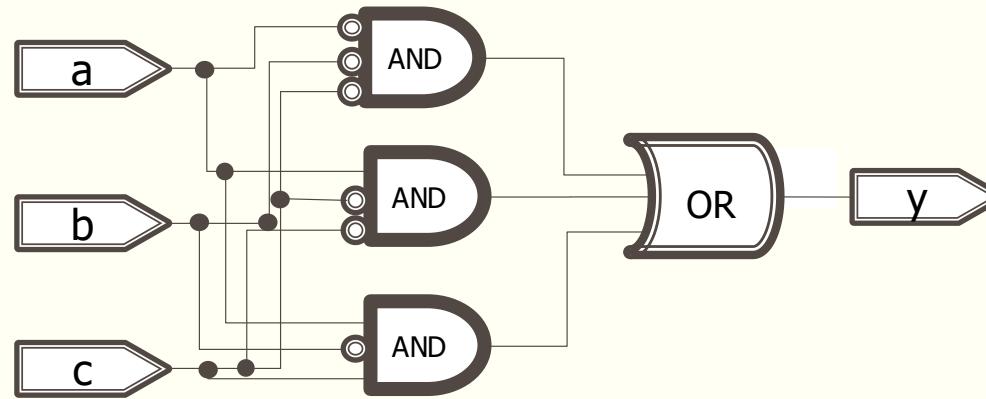

# A Note on Hardware Synthesis

---

One of the most common mistakes for beginners is to think of HDL as a computer program rather than as a shorthand for describing digital hardware. If you don't know approximately what hardware your HDL should synthesize into, you probably won't like what you get. You might create far more hardware than is necessary, or you might write code that simulates correctly but cannot be implemented in hardware. Instead, think of your system in terms of blocks of combinational logic, registers, and finite state machines. Sketch these blocks on paper and show how they are connected before you start writing code.

**Read H&H Chapter 4.1**

# What We Have Seen So Far

---

- Describing structural hierarchy with Verilog
  - Instantiate modules in an other module
- Describing functionality using behavioral modeling
- Writing simple logic equations
  - We can write AND, OR, XOR, ...
- Multiplexer functionality
  - If ... then ... else
- We can describe constants
- But there is more...

# More Verilog Examples

---

- We can write Verilog code in many different ways
- Let's see how we can express the same functionality by developing Verilog code
  - At a low-level of abstraction
    - Poor readability
    - Easier automated optimization (especially for low-level tools)
  - At a high-level of abstraction
    - Better readability
    - More difficult automated optimization (large search space)

# Comparing Two Numbers

---

- Defining your own gates as new modules
- We will use our gates to show different ways of implementing a 4-bit comparator (equality checker)

## *A 2-input XNOR gate*

```
module MyXnor (input A, B,  
                output Z);  
  
    assign Z = ~(A ^ B); //not XOR  
  
endmodule
```



## *A 2-input AND gate*

```
module MyAnd (input A, B,  
                output Z);  
  
    assign Z = A & B;      // AND  
  
endmodule
```
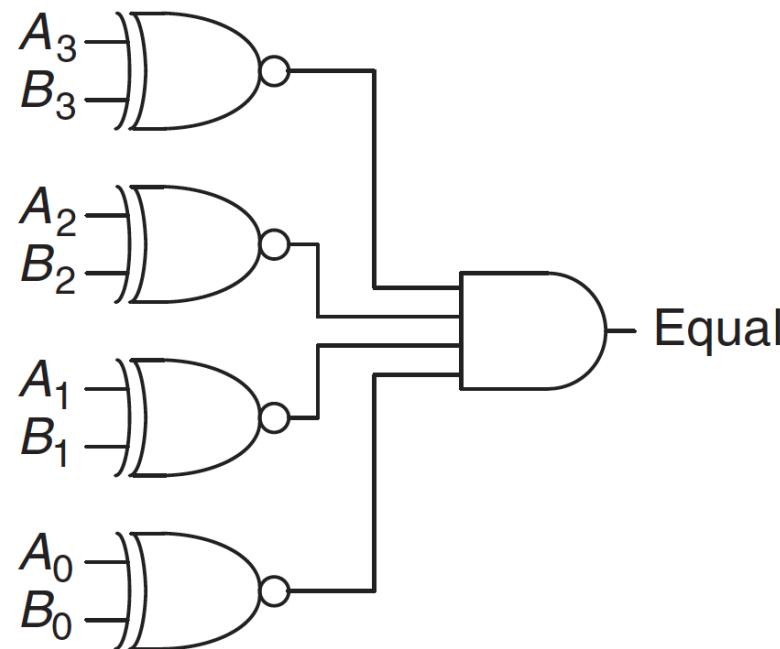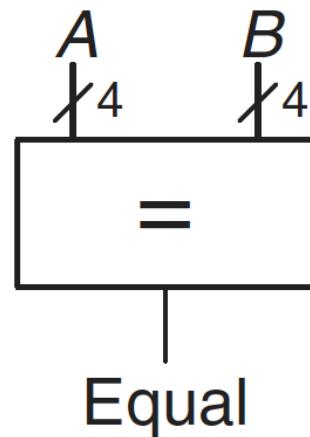
# Equality Checker (Compare if Equal)

---

- Checks if two N-input values are exactly the same
- Example: 4-bit Comparator



# Gate-Level Implementation

---

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
                output eq);
    wire c0, c1, c2, c3, c01, c23;

    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR
    MyAnd haha (.A(c0), .B(c1), .Z(c01) ); // AND
    MyAnd hoho (.A(c2), .B(c3), .Z(c23) ); // AND
    MyAnd bubu (.A(c01), .B(c23), .Z(eq) ); // AND

endmodule
```

# Using Logical Operators

---

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
                output eq);
    wire c0, c1, c2, c3, c01, c23;

    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR
    assign c01 = c0 & c1;
    assign c23 = c2 & c3;
    assign eq  = c01 & c23;

endmodule
```

# Eliminating Intermediate Signals

---

```
module compare (input a0, a1, a2, a3, b0, b1, b2, b3,
                output eq);
    wire c0, c1, c2, c3;

    MyXnor i0 (.A(a0), .B(b0), .Z(c0) ); // XNOR
    MyXnor i1 (.A(a1), .B(b1), .Z(c1) ); // XNOR
    MyXnor i2 (.A(a2), .B(b2), .Z(c2) ); // XNOR
    MyXnor i3 (.A(a3), .B(b3), .Z(c3) ); // XNOR
    // assign c01 = c0 & c1;
    // assign c23 = c2 & c3;
    // assign eq  = c01 & c23;
    assign eq  = c0 & c1 & c2 & c3;

endmodule
```

# Multi-Bit Signals (Bus)

---

```
module compare (input [3:0] a, input [3:0] b,
                output eq);
    wire [3:0] c; // bus definition

    MyXnor i0 (.A(a[0]), .B(b[0]), .Z(c[0])); // XNOR
    MyXnor i1 (.A(a[1]), .B(b[1]), .Z(c[1])); // XNOR
    MyXnor i2 (.A(a[2]), .B(b[2]), .Z(c[2])); // XNOR
    MyXnor i3 (.A(a[3]), .B(b[3]), .Z(c[3])); // XNOR

    assign eq = &c; // short format

endmodule
```

# Bitwise Operations

---

```
module compare (input [3:0] a, input [3:0] b,
                output eq);
    wire [3:0] c; // bus definition

    // MyXnor i0 (.A(a[0]), .B(b[0]), .Z(c[0]) );
    // MyXnor i1 (.A(a[1]), .B(b[1]), .Z(c[1]) );
    // MyXnor i2 (.A(a[2]), .B(b[2]), .Z(c[2]) );
    // MyXnor i3 (.A(a[3]), .B(b[3]), .Z(c[3]) );

    assign c = ~(a ^ b); // XNOR

    assign eq = &c; // short format

endmodule
```

# Highest Abstraction Level: Comparing Two Numbers

---

```
module compare (input [3:0] a, input [3:0] b,
                output eq);

    // assign c = ~(a ^ b); // XNOR

    // assign eq = &c; // short format

    assign eq = (a == b) ? 1 : 0; // really short

endmodule
```

# Writing More Reusable Verilog Code

---

- We have a module that can compare two 4-bit numbers
- What if in the overall design we need to compare:
  - 5-bit numbers?
  - 6-bit numbers?
  - ...
  - N-bit numbers?
  - Writing code for each case looks tedious
- What could be a better way?

# Parameterized Modules

---

In Verilog, we can define module parameters

```
module mux2
  #(parameter width = 8) // name and default value
  (input [width-1:0] d0, d1,
   input             s,
   output [width-1:0] y);

  assign y = s ? d1 : d0;
endmodule
```

We can set the parameters to different values  
when instantiating the module

# Instantiating Parameterized Module

---

```
module mux2
#(parameter width = 8) // name and default value
(input [width-1:0] d0, d1,
 input s,
 output [width-1:0] y);

assign y = s ? d1 : d0;
endmodule
```



# What about Timing?

---

- It is possible to define *timing relations* in Verilog. **BUT:**
  - These are **ONLY** for simulation
  - They **CAN NOT** be synthesized
  - They are used for *modeling delays* in a circuit

```
'timescale 1ns/1ps
module simple (input a, output z1, z2);

assign #5 z1 = ~a; // inverted output after 5ns
assign #9 z2 = a; // output after 9ns

endmodule
```

**More on this soon**

# Good Practises

---

- Develop/use a **consistent** naming style
  
- Use **MSB to LSB ordering** for buses
  - Use “**a[31:0]**”, **not “a[0:31]”**
  
- Define **one module per file**
  - Makes managing your design hierarchy easier
  
- Use a file name that matches module name
  - e.g., module **TryThis** is defined in a file called **TryThis.v**
  
- Always keep in mind that **Verilog describes hardware**

# Summary (HDL for Combinational Logic)

---

- We have seen an overview of Verilog
- Discussed structural and behavioral modeling
- Studied combinational logic constructs